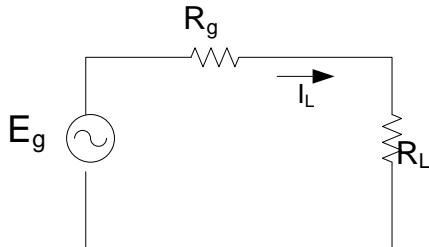


## Wind Generator Circuit Power Analysis

The following is the equivalent circuit for a wind turbine.

$E_g$  is the open circuit voltage with  $R_L$  open.

$R_g$  = the internal generator resistance



Using Ohms law the current  $I_L$  is:

$$I_L = E_g / (R_g + R_L)$$

The total circuit power is:

$$P_T = P_g + P_L = I_L^2 R_g + I_L^2 R_L = I_L^2 (R_g + R_L)$$

Substituting for  $I_L$ :

$$P_T = (E_g / (R_g + R_L))^2 (R_g + R_L) = E_g^2 / (R_g + R_L)$$

From the generator equation:

$$E_g = 0.707.PBNAZ$$

For the 4-Pole generator design with typical parameter values:

$P = 4$  poles,  $B = 0.12$  T,  $N = 800$  turns,  $A = 0.001$ m-sq,  $Z = \text{rps} = \text{rpm}/60$

$$K_E = 0.707.PBNA = 0.005 \text{ volts / rpm}$$

Substitute  $E_g$  :

$$P_T = K_E^2 / (R_g + R_L) (\text{rpm})^2$$

Example:

$R_g = 13$  ohms ,  $R_L = 15$  ohm, rpm = 600,  $K_E = 0.005$

$$P_T = (0.005)^2 (600)^2 / (13 + 15) = 0.3214 \text{ watts}$$